

# HARDWARE FOR ARITHMETIC

Mahdi Nazm Bojnordi

Assistant Professor

School of Computing



University of Utah

# Overview

- Homework is due on Mar. 5<sup>th</sup>
  - ▣ after conversion to binary and normalization, we may end up with too many bits for F
- This lecture
  - ▣ Basics of logic design
  - ▣ Hardware for arithmetic

  
# Fundamentals of Digital Design

- **Binary logic:** two voltage levels
  - ▣ high and low; 1 and 0; true and false
- **Binary arithmetic**
  - ▣ Based on a 3-terminal device that acts as a switch


 
# Logic Blocks


- A logic block comprises binary inputs and binary outputs
  - ▣ **Combinational**: the output is only a function of the inputs
  - ▣ **Sequential**: the block has some internal memory (state) that also influences the output
- **Gate**: a basic logic block that implements AND, OR, NOT, etc.



# Logic Blocks: Truth Table

- A **truth table** defines the outputs of a logic block for each set of inputs
- ▣ **Example:** consider a block with 3 inputs A, B, C and an output E that is true only if exactly 2 inputs are true

A	B	C	E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

 

# Boolean Algebra

- Three primary operators are used to realize Boolean functions
  
- Boolean operations
  - ▣ OR (symbol  $+$ )
    - $X = A + B$  :  $X$  is true if at least one of  $A$  or  $B$  is true
  - ▣ AND (symbol  $.$ )
    - $X = A . B$  :  $X$  is true if both  $A$  and  $B$  are true
  - ▣ NOT (symbol  $\overline{\phantom{x}}$ )
    - $X = \overline{A}$  :  $X$  is the inverted value of  $A$

# Pictorial Representation

- Logic gates


AND



OR



NOT

 

- What function is the following?



# Boolean Algebra Rules

## □ Identity law

- ▣  $A + 0 = A$

- ▣  $A \cdot 1 = A$

## □ Commutative laws

- ▣  $A + B = B + A$

- ▣  $A \cdot B = B \cdot A$

## □ Zero and One laws

- ▣  $A + 1 = 1$

- ▣  $A \cdot 0 = 0$

## □ Associative laws

- ▣  $A + (B + C) = (A + B) + C$

- ▣  $A \cdot (B \cdot C) = (A \cdot B) \cdot C$

## □ Inverse laws

- ▣  $A \cdot \overline{A} = 0$

- ▣  $A + \overline{A} = 1$

## □ Distributive laws


- ▣  $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$

- ▣  $A + (B \cdot C) = (A + B) \cdot (A + C)$



 
# DeMorgan's Law


□  $\overline{A + B} = \overline{A} \cdot \overline{B}$




=

 

 □  $\overline{A \cdot B} = \overline{A} + \overline{B}$



=

 

# Example: Boolean Equation

- Consider the logic block that has an output E that is true only if exactly two of the three inputs A, B, C are true
- Multiple correct equations
  - Two must be true, but all three cannot be true
    - $E = ((A \cdot B) + (B \cdot C) + (A \cdot C)) \cdot \overline{(A \cdot B \cdot C)}$
  - Identify the three cases where it is true
    - $E = (A \cdot B \cdot \overline{C}) + (A \cdot C \cdot \overline{B}) + (C \cdot B \cdot \overline{A})$

# Implementing Boolean Functions

- Can realize any logic block with the AND, OR, NOT
  - ▣ Draw the truth table
  - ▣ For each true output, represent the corresponding inputs as a product
  - ▣ The final equation is a sum of these products

A	B	C	E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

# Implementing Boolean Functions

- Can realize any logic block with the AND, OR, NOT
  - ▣ Draw the truth table
  - ▣ For each true output, represent the corresponding inputs as a product
  - ▣ The final equation is a sum of these products

A	B	C	E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$\overline{A}.B.C$

$A.\overline{B}.C$

$A.B.\overline{C}$

# Implementing Boolean Functions

- Can realize any logic block with the AND, OR, NOT
  - ▣ Draw the truth table
  - ▣ For each true output, represent the corresponding inputs as a product
  - ▣ The final equation is a sum of these products

A	B	C	E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0


$\bar{A}.B.C$

$A.\bar{B}.C$

$A.B.\bar{C}$

Sum of Products
 
$$E = (\bar{A}.B.C) + (A.\bar{B}.C) + (A.B.\bar{C})$$




# Universal Gates

- Universal gate is a logic that can be used to implement any complex function


- NAND

 - Not of AND
- $A \text{ nand } B = \overline{A.B}$




- NOR

 - Not of OR
- $A \text{ nor } B = \overline{A+B}$


 
# Common Logic Block



- An n-input **decoder** takes n inputs, based on which only one out of  $2^n$  outputs is activated



$I_0$	$I_1$	$I_2$	$O_0$	$O_1$	$O_2$	$O_3$	$O_4$	$O_5$	$O_6$	$O_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1
  
# Common Logic Block

- A **multiplexer (or selector)** reflects one of  $n$  inputs on the output depending on the value of the select bits
  - ▣ Example: 2-input mux





# Common Logic Block

- A **full adder** generates the sum and carry for each bit position

A	B	C <sub>in</sub>	Sum	C <sub>out</sub>
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

1	0	0	1
0	1	0	1

---

Sum  
Cout

# Common Logic Block

- A **full adder** generates the sum and carry for each bit position

A	B	C <sub>in</sub>	Sum	C <sub>out</sub>
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

	1	0	0	1
	0	1	0	1
Sum	1	1	1	0
Cout	0	0	0	1

# Common Logic Block

- A **full adder** generates the sum and carry for each bit position

A	B	C <sub>in</sub>	Sum	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

	1	0	0	1
	0	1	0	1
Sum	1	1	1	0
Cout	0	0	0	1


## Equations:

$$\text{Sum} = C_{in} \cdot \overline{A} \cdot \overline{B} + B \cdot \overline{C}_{in} \cdot \overline{A} + A \cdot \overline{C}_{in} \cdot \overline{B} + A \cdot B \cdot C_{in}$$

$$\begin{aligned} \text{Cout} = & A \cdot B \cdot C_{in} + A \cdot B \cdot \overline{C}_{in} + A \cdot C_{in} \cdot \overline{B} + B \cdot C_{in} \cdot \overline{A} = \\ & A \cdot B + A \cdot C_{in} + B \cdot C_{in} \end{aligned}$$
 
# Common Logic Block

- A **full adder** generates the sum and carry for each bit position



	1	0	0	1
	0	1	0	1
Sum	1	1	1	0
Cout	0	0	0	1

## Equations:

$$\text{Sum} = C_{in} \cdot \bar{A} \cdot \bar{B} + B \cdot \bar{C}_{in} \cdot \bar{A} + A \cdot \bar{C}_{in} \cdot \bar{B} + A \cdot B \cdot C_{in}$$

$$\begin{aligned} \text{Cout} = & A \cdot B \cdot C_{in} + A \cdot B \cdot \bar{C}_{in} + A \cdot C_{in} \cdot \bar{B} + B \cdot C_{in} \cdot \bar{A} = \\ & A \cdot B + A \cdot C_{in} + B \cdot C_{in} \end{aligned}$$