

# CPU ORGANIZATION

Mahdi Nazm Bojnordi

Assistant Professor

School of Computing

University of Utah

# Overview

---

- Notes

- ▣ Homework 7 is due tonight

- Verify your submitted file before midnight


- This lecture

- ▣ Finite state machine

- ▣ Central processing unit

 
# Recall: Design of an S-R Latch

- An S-R latch: set-reset latch
  - ▣ When Set is high, a 1 is stored
  - ▣ When Reset is high, a 0 is stored
  - ▣ When both are low, the previous state is preserved (hence, known as a storage or memory element)
  - ▣ Both are high – this set of inputs is not allowed


 
# Design of a D Latch


- The value of the input D signal (data) is stored only when the clock is high – the previous state is preserved when the clock is low



# Design of a D Flip Flop

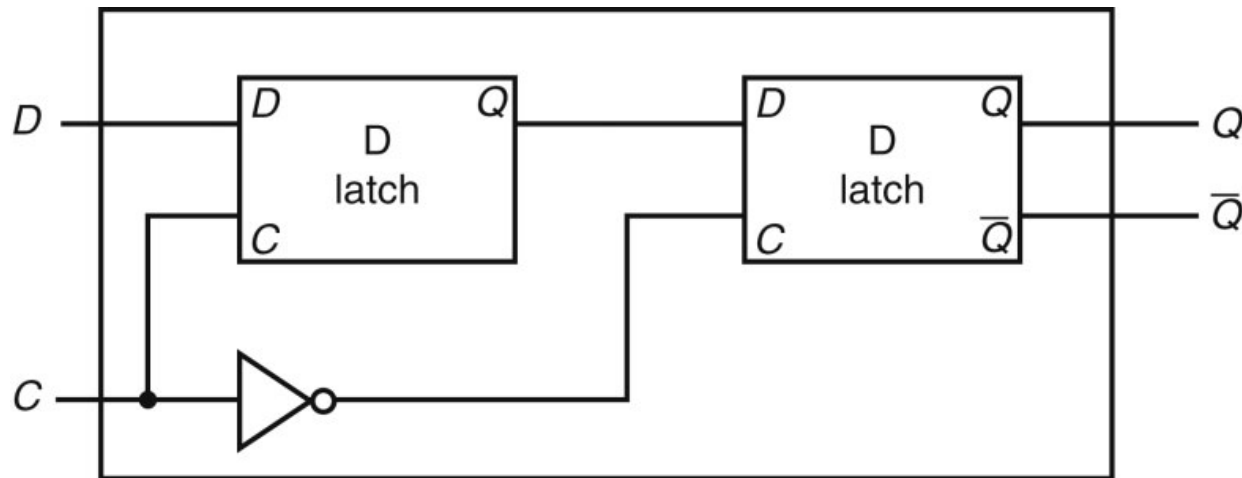
## □ Latch vs. Flip Flop

- Latch: outputs can change any time the clock is high (asserted)
- Flip flop: outputs can change only on a clock edge
  - Technically, two D latches in series


 
# State Diagram


- Each state is shown with a circle, labeled with the state value
  - ▣ the contents of the circle are the outputs
- An arc represents a transition to a different state, with the inputs indicated on the label



What is this state diagram for?
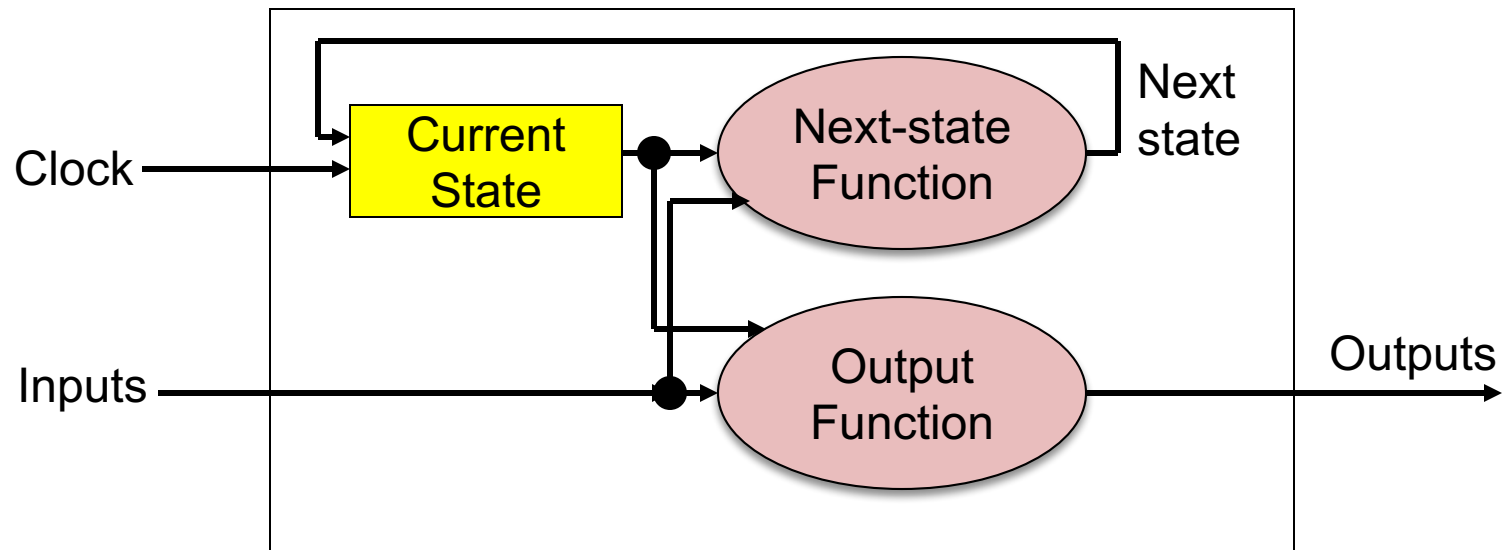
# Finite State Machine

- A sequential circuit is described by a finite state diagram.
  - ▣ We use variation of a truth table for inputs and outputs
  - ▣ Note that state is updated only on a clock edge




# Example: Counters

- Counters are an important class of finite state machines
- **Design:** a circuit that stores a 3-bit number and increments the value on every clock edge.
  - ▣ It starts again from 0 when reaching the largest value.
  - ▣ Draw the state diagram; how many states and inputs?


 
# Example: Counters

- Counters are an important class of finite state machines
- **Design:** a circuit that stores a 3-bit number and increments the value on every clock edge.
  - ▣ It starts again from 0 when reaching the largest value.
  - ▣ Draw the state diagram; how many states and inputs?



# Example: Traffic Control Light

- A traffic light with only green and red; either the North-South road has green or the East-West road has green (both can't be red).
- **Design:** there are detectors on the roads to indicate if a car is on the road; the lights are updated every 30 seconds; a light need change only if a car is waiting on the other road
  - ▣ How many inputs, outputs, and states?

# Example: Traffic Control Light


- A traffic light with only green and red; either the North-South road has green or the East-West road has green (both can't be red).
- **Design:** there are detectors on the roads to indicate if a car is on the road; the lights are updated every 30 seconds; a light need change only if a car is waiting on the other road
  - ▣ How many inputs, outputs, and states?

## State Transition Table:

CurrState	InputEW	InputNS	NextState=Output
N	0	0	N
N	0	1	N
N	1	0	E
N	1	1	E
E	0	0	E
E	0	1	N
E	1	0	E
E	1	1	N
 
# Example: Traffic Control Light

- A traffic light with only green and red; either the North-South road has green or the East-West road has green (both can't be red).
- **Design:** there are detectors on the roads to indicate if a car is on the road; the lights are updated every 30 seconds; a light need change only if a car is waiting on the other road
  - ▣ How many inputs, outputs, and states?




# A Simple Processor

- What do we need for a basic MIPS processor?
  - ▣ basic math (add, sub, and, or, slt)
  - ▣ memory access (lw and sw)
  - ▣ branch and jump instructions (beq and j)
- Main components
  - ▣ Memory
    - Data and instructions
  - ▣ Register, ALU, and control logic
  - ▣ Common operations
    - Fetch unit
    - Register read
 
# Overview of the Processor

- What is the role of the Add units?
- Explain the inputs to the data memory unit
- Explain the inputs to the ALU
- Explain the inputs to the register unit



# Clocking the Processor

- Which of the units need a clock?
- What is being saved (latched) on the rising edge of the clock?
- Keep in mind that the latched value remains there for an entire cycle

