

ARITHMETIC AND LOGIC UNIT

Mahdi Nazm Bojnordi

Assistant Professor

School of Computing

University of Utah

Overview

- Notes

- ▣ Homework is due tonight

- Verify your submitted file before midnight

- ▣ No lecture on Thursday

- Instead, a review on common mistakes and questions by the TAs

- This lecture


- ▣ How to build an arithmetic and logic unit (ALU)

Recall: Common Logic Block

- Any Boolean function can be represented by a **truth table** and **sum of products** (two gate levels)
- An n-input **decoder** takes n inputs, based on which only one out of 2^n outputs is activated
- A **multiplexer (or selector)** reflects one of n inputs on the output depending on the value of the select bits
- A **full adder** generates the sum and carry for each bit position


Multi-Function Blocks

 - A 1-bit ALU with ADD, OR, and AND operations
 - ▣ A multiplexer selects between the operations




Multibit ALU

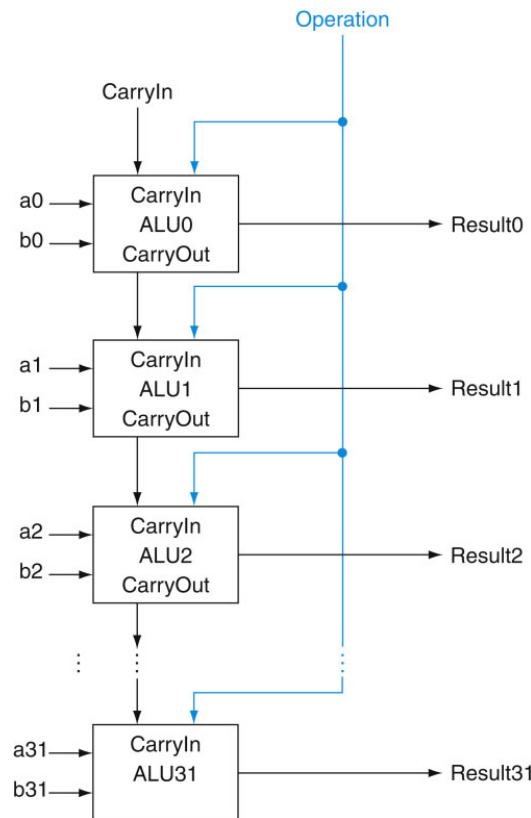- 1-bit ALUs are connected “in series” with the carry-out of 1 box going into the carry-in of the next box




Incorporating Subtraction

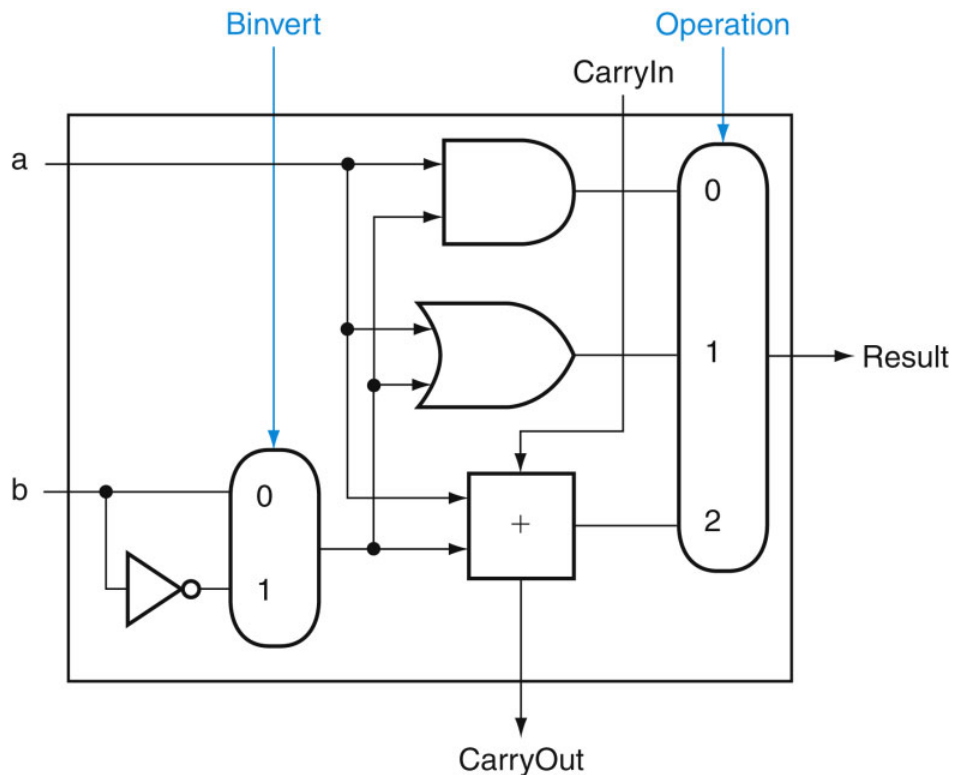- Must invert bits of B and add a 1
 - ▣ Include an inverter **CarryIn** for the first bit is 1
- The **CarryIn** signal (for the first bit) can be the same as the **Binvert** signal




Incorporating NAND and NOR

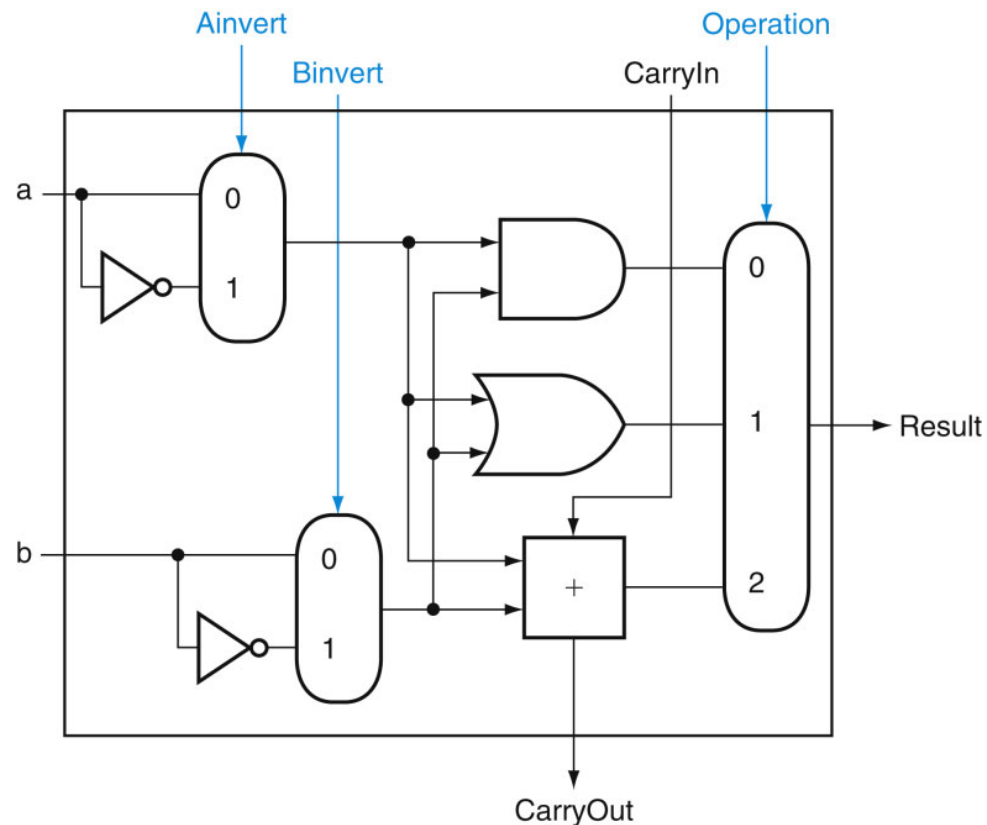- Must invert bits of A and B to realize NAND and NOR
 - ▣ Recall DeMorgan's Laws



Incorporating Comparison

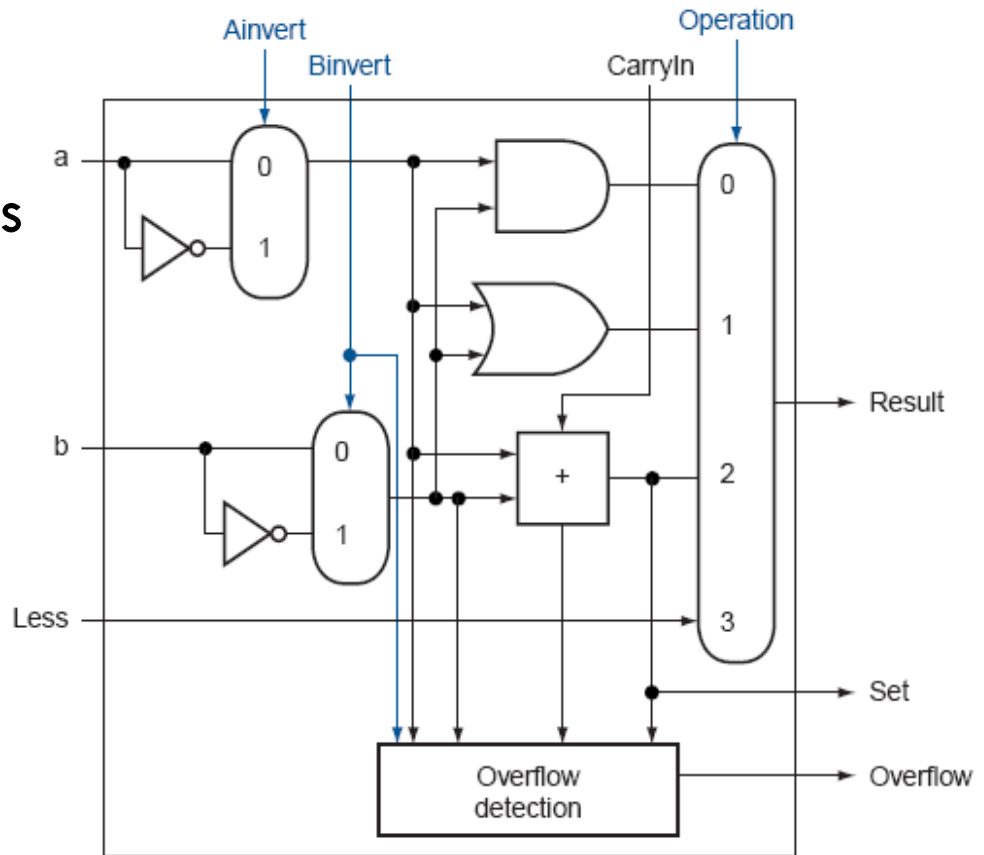- For example: the **slt** instruction
 - ▣ Perform $a - b$ and check the sign
 - ▣ New signal (Less) that is zero for ALU boxes 1 - 31
 - ▣ The 31st box has a unit to detect overflow and sign – the sign bit serves as the Less signal for the 0th box




Incorporating Comparison

□ For example: the **beq** instruction

■ Perform $a - b$ and confirm that the result is all zero's

■ What about **bne**?

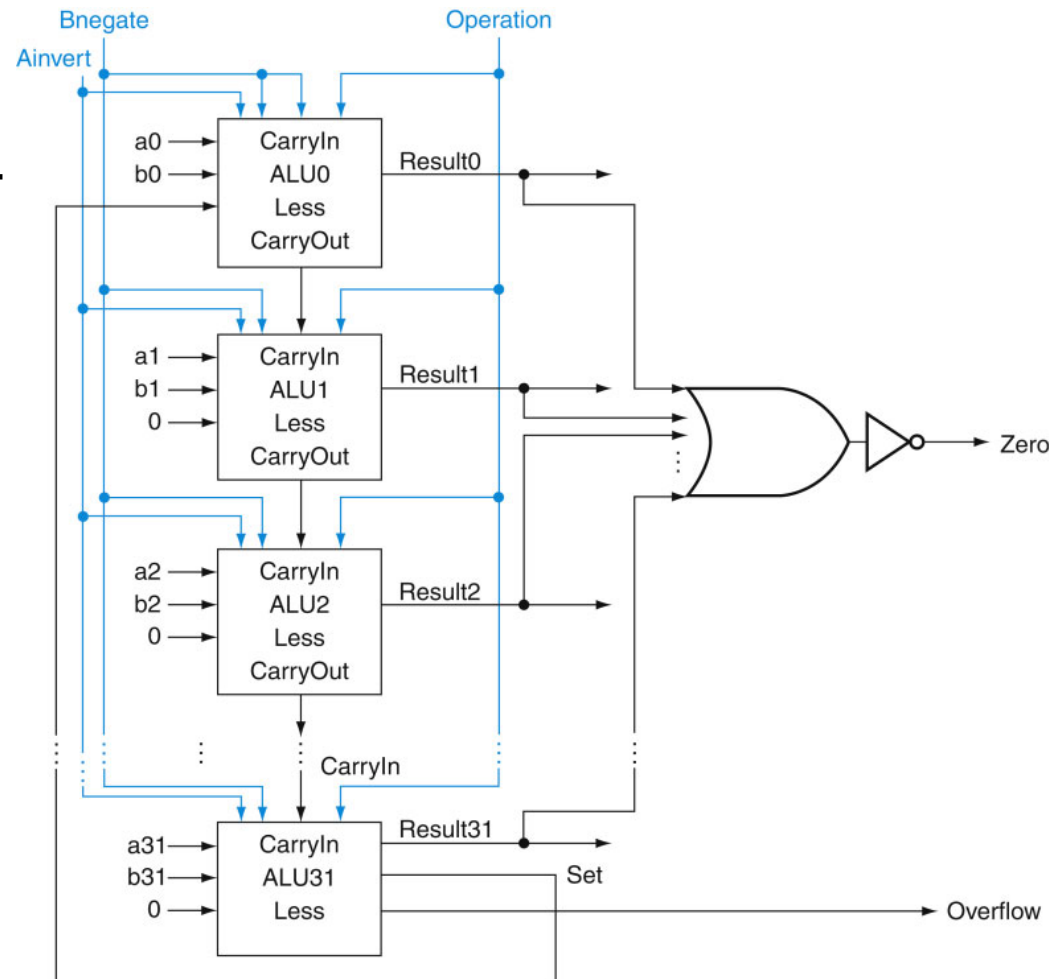■ Control lines determine what operations to be done.



Incorporating Comparison


□ For example: the **beq** instruction

▣ Perform $a - b$ and confirm that the result is all zero's

▣ **What about bne?**


▣ Control lines determine what operations to be done.

	Ai	Bn	Op
AND	0	0	00
OR	0	0	01
Add	0	0	10
Sub	0	1	10
SLT	0	1	11
NOR	1	1	00

 

Carry Ripple Adder

 - Simplest design by cascading 1-bit boxes
 - ▣ Each 1-bit box sequentially implements AND and OR
 - ▣ Critical path: the total delay is the time to go through 64 gates
- How to make a 32-bit addition faster?



Carry Ripple Adder

- Simplest design by cascading 1-bit boxes
 - ▣ Each 1-bit box sequentially implements AND and OR
 - ▣ Critical path: the total delay is the time to go through 64 gates
- How to make a 32-bit addition faster?
- **Recall:** any logic equation can be expressed as the sum of products (only 2 gate levels!)
 - ▣ Challenges: many parallel gates with very large inputs
 - ▣ **Solution:** we'll find a compromise

Fast Adder

- Computing carry-outs

- ▣ $\text{CarryIn1} = b0.\text{CarryIn0} + a0.\text{CarryIn0} + a0.b0$

- ▣ $\text{CarryIn2} = b1.\text{CarryIn1} + a1.\text{CarryIn1} + a1.b1$

- ▣ $\quad\quad\quad = b1.b0.c0 + b1.a0.c0 + b1.a0.b0 +$

- ▣ $\quad\quad\quad a1.b0.c0 + a1.a0.c0 + a1.a0.b0 + a1.b1$

- ▣ ...

- ▣ $\text{CarryIn32} = \text{a really large sum of really large products}$

- Each gate is enormous and slow!

Fast Adder

- Computing carry-outs: equation re-phrased
- $C_{i+1} = a_i.b_i + a_i.C_i + b_i.C_i$
- $= (a_i.b_i) + (a_i + b_i).C_i$

- Generate signal $= a_i.b_i$
 - The current pair of bits will generate a carry if they are both 1
- Propagate signal $= a_i + b_i$
 - The current pair of bits will propagate a carry if either is 1

- Therefore, $C_{i+1} = G_i + P_i . C_i$

Fast Adder

□ Computing carry-outs: example

$$c1 = g0 + p0.c0$$

$$c2 = g1 + p1.c1 = g1 + p1.g0 + p1.p0.c0$$

$$c3 = g2 + p2.g1 + p2.p1.g0 + p2.p1.p0.c0$$

$$c4 = g3 + p3.g2 + p3.p2.g1 + p3.p2.p1.g0 + p3.p2.p1.p0.c0$$

(1) (2) (3) (4) (4)


Either,

- (1) a carry was just generated, or
- (2) a carry was generated in the last step and was propagated, or
- (3) a carry was generated two steps back and was propagated by both the next two stages, or
- (4) a carry was generated N steps back and was propagated by every single one of the N next stages

Fast Adder

□ Divide and Conquer

 - **Challenge:** for the 32nd bit, we must AND every single propagate bit to determine what becomes of c0 (among other things)
- **Solution:** the bits are broken into groups (of 4) and each group computes its group-generate and group-propagate
- For example, to add 32 numbers, you can partition the task as a tree



Fast Adder

- P and G for 4-bit blocks
 - Compute P0 and G0 (super-propagate and super-generate) for the first group of 4 bits (and similarly for other groups of 4 bits)
 - $P0 = p0.p1.p2.p3$
 - $G0 = g3 + g2.p3 + g1.p2.p3 + g0.p1.p2.p3$
 - Carry out of the first group of 4 bits is
 - $C1 = G0 + P0.c0$
 - $C2 = G1 + P1.G0 + P1.P0.c0$
 - $C3 = G2 + (P2.G1) + (P2.P1.G0) + (P2.P1.P0.c0)$
 - $C4 = G3 + (P3.G2) + (P3.P2.G1) + (P3.P2.P1.G0) + (P3.P2.P1.P0.c0)$
- By having a tree of sub-computations, each AND, OR gate has few inputs and logic signals have to travel through a modest set of gates (equal to the height of the tree)

Fast Adder

□ Example

Add	A	0001	1010	0011	0011
	B	1110	0101	1110	1011
	g	0000	0000	0010	0011
	p	1111	1111	1111	1011

P	1	1	1	0
G	0	0	1	0

C4 = 1

Fast Adder: Carry Look-Ahead

- 16-bit Ripple-carry takes 32 steps
- This design takes how many steps?

